

$$= 50 + 90 \cos(100t - 90^\circ) \text{ V}$$

6-1. 如图 1 所示电路, $u_s = 50 + 90 \sin(100t) \text{ V}$, $i_s = 20 \cos(50t) \text{ A}$ 。试计算: (1) 稳态响应 i_L 、 u_C ; (2) 电压源提供的有功功率。


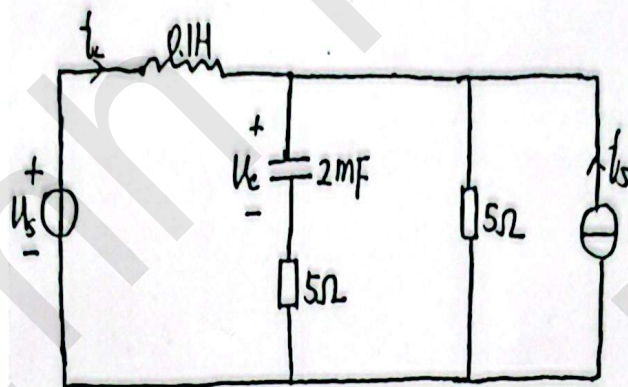


图 1

1) 直流量作用, $I_{L0} = \frac{50}{5} = 10 \text{ A}$, $V_{C0} = 50 \text{ V}$

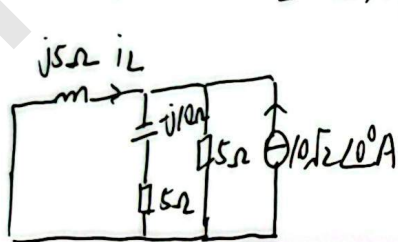2) 基波分量作用时, $X_L = 5 \Omega$, $X_C = \frac{1}{\omega C} = 10 \Omega$



$$\dot{I}_{L1} = - \frac{\frac{1}{j5}}{\frac{1}{5} + \frac{1}{5-j10} + \frac{1}{j5}} \times 10\sqrt{2} \angle 0^\circ = 10.5538 \angle 116.57^\circ \text{ A (分流公式)}$$

$$\dot{V}_{C1} = \frac{\frac{1}{5-j10}}{\frac{1}{5} + \frac{1}{5-j10} + \frac{1}{j5}} \cdot (-j10) \cdot 10\sqrt{2} \angle 0^\circ = 47.19 \angle 0^\circ \text{ V}$$

3) $\omega = 100 \text{ rad/s}$ 时, $X_L = 10 \Omega$, $X_C = 5 \Omega$

$$\dot{I}_{L2} = \frac{45\sqrt{2} \angle -90^\circ}{j10 + \frac{(5-j5) \times 5}{10-j5}} = \frac{45\sqrt{2} \angle -90^\circ}{3+j9} = 6.7082 \angle -161.57^\circ \text{ A}$$

$$\dot{V}_{C2} = 6.7082 \angle -161.57^\circ \times \frac{5}{10-j5} \times (-j5) = 15 \angle 135^\circ \text{ V (将 } \dot{I}_{L2} \text{ 分流再乘以容抗)}$$

$$i_L = [10 + 14.93 \cos(50t + 116.57^\circ) + 9.49 \cos(100t - 161.57^\circ)] \text{ A}$$

$$u_C = [50 + 66.74 \cos(50t) + 21.21 \cos(100t + 135^\circ)] \text{ V}$$

(2) $P = 50 \times 10 + \frac{9.49 \times 90}{2} \cos(-90^\circ + 161.57^\circ) = 635 \text{ W}$

6-2. 如图 2 所示电路, 已知

$$R = 10\Omega, \omega L = 2\Omega, \frac{1}{\omega C} = 18\Omega, u_s = 10 + 8\sqrt{2}\cos(\omega t) + 12\sqrt{2}\cos(3\omega t + 30^\circ)\text{V},$$

$$i_s = 5\sqrt{2}\cos(\omega t + 60^\circ)\text{A}. \text{求电流表的读数以及两电源各自发出的功率}$$

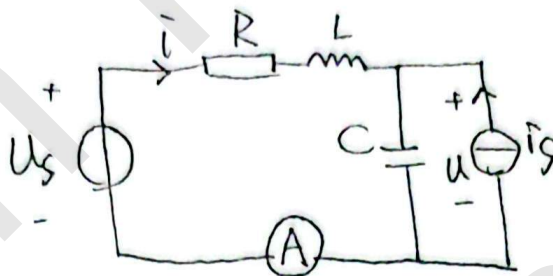


图 2

① 直流作用, $I_0 = 0\text{A}$, $U_0 = 10\text{V}$

② 基波单独作用, 由叠加定理有, u_s 和 i_s 分别单独作用

$$\dot{I}_1 = \frac{8\angle 0^\circ}{10 - j16} - \frac{j18}{10 - j16} \times 5\angle 60^\circ = 4.4079\angle -154.77^\circ\text{A}$$

$$\dot{U}_1 = (\dot{I}_1 + \dot{I}_s) \times (-j18) = \cancel{5} (4.4079\angle -154.77^\circ + 5\angle 60^\circ) \times 18\angle -90^\circ = 51.61\angle 31.25^\circ\text{V}$$

$$\text{③ 三次谐波作用时, } \dot{I}_3 = \frac{12\angle 30^\circ}{10} = 1.2\angle 30^\circ\text{A}$$

$$\text{读数 } I = \sqrt{I_1^2 + I_3^2} = 4.568\text{A}$$

$$P_{u_s} = 8 \times 4.4079 \times \cos(154.77^\circ) + 1.2 \times 12 = -17.5\text{W}$$

$$P_{i_s} = 51.61 \times 5 \times \cos(31.25^\circ - 60^\circ) = 226.24\text{W}$$

7-1. 如图3所示的正弦交流稳态电路, $M=10\text{mH}$, $L_1=10\text{mH}$, $L_2=40\text{mH}$, $C=4/3\mu\text{F}$ 。
已知电压源有效值 $U_s=50\text{V}$ 。试求: 电压源频率为多大时电流表的读数最小, 并求此最小值。


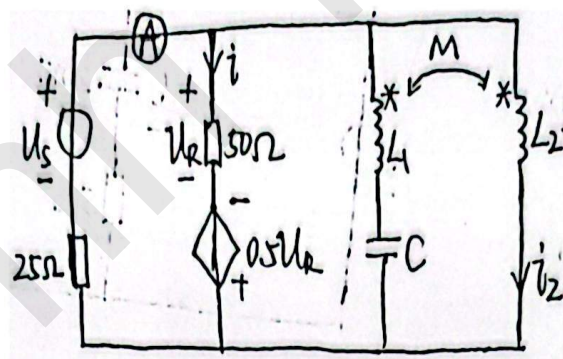


图3


右侧并联谐振时, 电流表读数最小

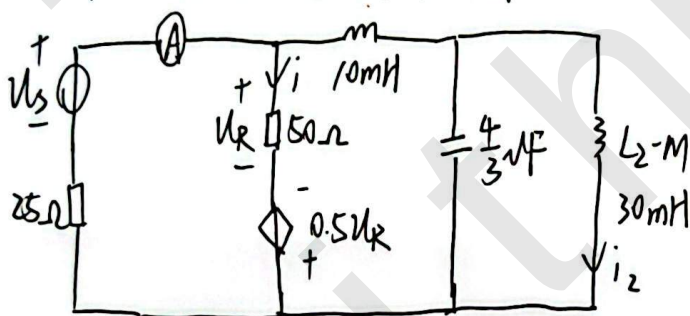

$$\omega(L_2 - M) = \frac{1}{\omega C}, \quad \omega = \sqrt{\frac{1}{(L_2 - M)C}} = 5000 \text{ rad/s}, \quad f = \frac{\omega}{2\pi} = 795.77 \text{ Hz}$$

$$\begin{cases} I = \frac{50 + 0.5U_R}{75} \\ U_R = 50I \end{cases} \Rightarrow I = 1 \text{ A}$$

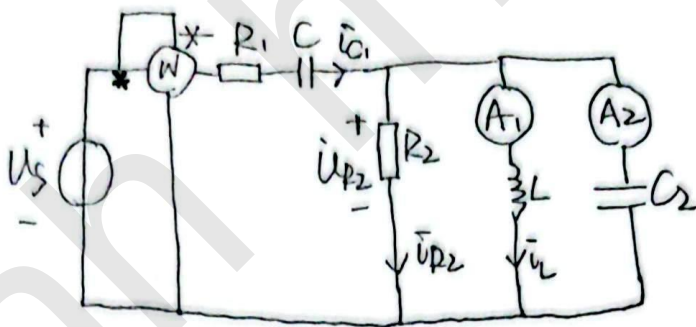7-2. 如图4所示电路处在谐振状态, $R_2 = 3\omega L = 2 \frac{1}{\omega C}$, $R_1 = 1\Omega$, $U_s = 20V$, 电流表 A_1 的读数是 $30A$, 求电流表 A_2 和功率表 W 的读书, 并求电容 C_2 的容抗



电感 L 支路. $\dot{I}_L = \frac{\dot{U}_{R2}}{j\omega L} = -j3 \frac{U_{R2}}{R_2} = -j3I_{R2}$

$I_L = 30A$. $\therefore I_{R2} = 10A$ 设 $I_{R2} = 10\angle 0^\circ$ $\dot{I}_L = 30\angle -90^\circ A$

$I_{C2} = I_{C2}\angle 90^\circ$ $\dot{I}_{C1} = 10 + j(I_{C2} - 30)$

等效阻抗: $Z = R_1 + \frac{1}{j\omega C} + \frac{\dot{U}_{R2}}{\dot{I}_{C1}}$
 $= R_1 - j\frac{R_2}{2} + \frac{10 - R_2}{10 + j(I_{C2} - 30)}$

$= R_1 + \frac{100R_2}{100 + (I_{C2} - 30)^2} - j\left[\frac{R_2}{2} + \frac{10R_2(I_{C2} - 30)}{100 + (I_{C2} - 30)^2}\right]$

$\therefore \frac{R_2}{2} + \frac{10R_2(I_{C2} - 30)}{100 + (I_{C2} - 30)^2} = 0$ $\therefore I_{C2} = 20A$

$\dot{I}_{C2} = 20\angle 90^\circ$ $\dot{I}_{C1} = 10 - j10 = 10\sqrt{2}\angle -45^\circ A$

$\dot{U}_s = (10 - j10)\left(1 + \frac{1}{j\omega C}\right) + 10R_2$ $U_s = 20V$ $R_2 = (2\sqrt{2} - 2)\Omega$

$P = I_{C1}^2 R_1 + I_{R2}^2 R_2 = 282.8W$

$X_{C2} = \frac{I_{R2} R_2}{I_{C2}} = 0.414\Omega$