
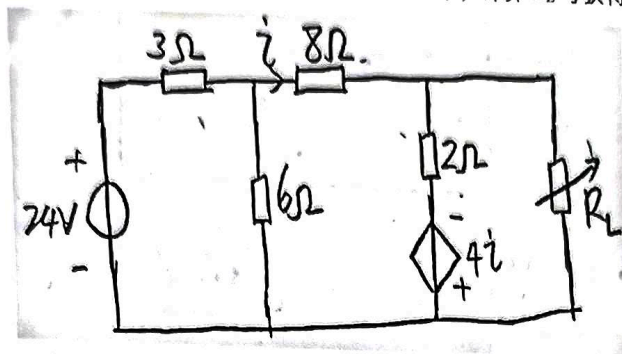


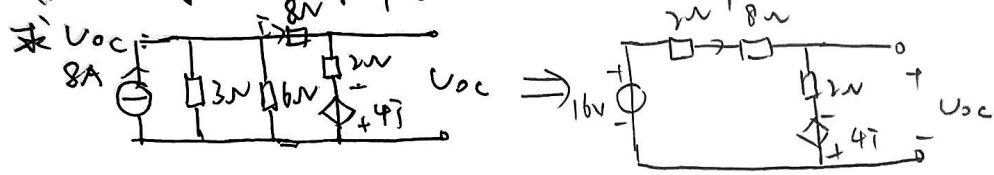
1. 如图 3-1 所示电路, (1) R_L 为何值时, 可获得最大功率; (2) 计算 R_L 可获得的最大功率。



对 R_L 左侧电路戴维南等效:


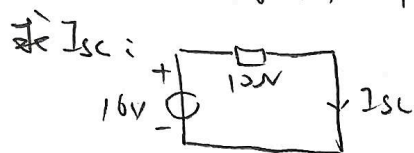
$$16 - 10\bar{i} = -4\bar{i} + 2\bar{i} \quad \bar{i} = 2A \quad U_{OC} = -4V$$





$$I_{SC} = 1.6A$$

$$R_i = \frac{U_{OC}}{I_{SC}} = 2.5\Omega$$



$$R_L = R_i = 2.5\Omega \text{ 时}$$

$$P_{max} = \frac{U_{OC}^2}{4R_L} = 1.6W$$

2. 如图 3-2 所示电路, 计算电流 i 。

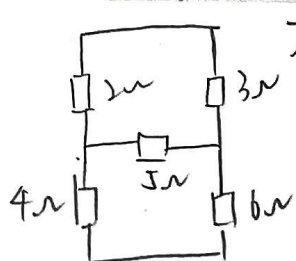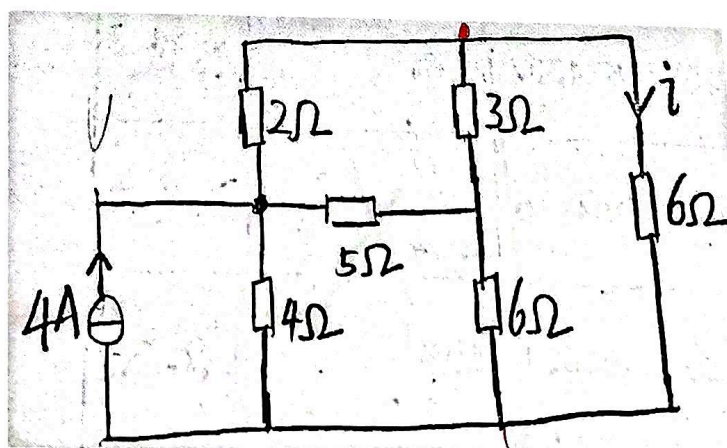


构成电桥: 5Ω 电阻相当于断路:

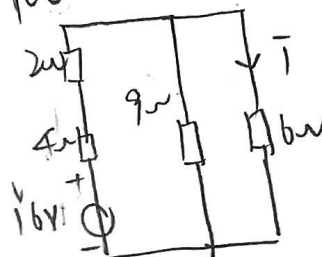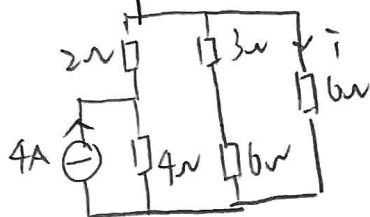


$$\bar{i} = \frac{16}{9 + 6 + 6} \times \frac{9}{9 + 6} = 1A$$

3. 试用戴维南定理求题图 3-3 所示电路中 ab 支路的电流 I_{ab}

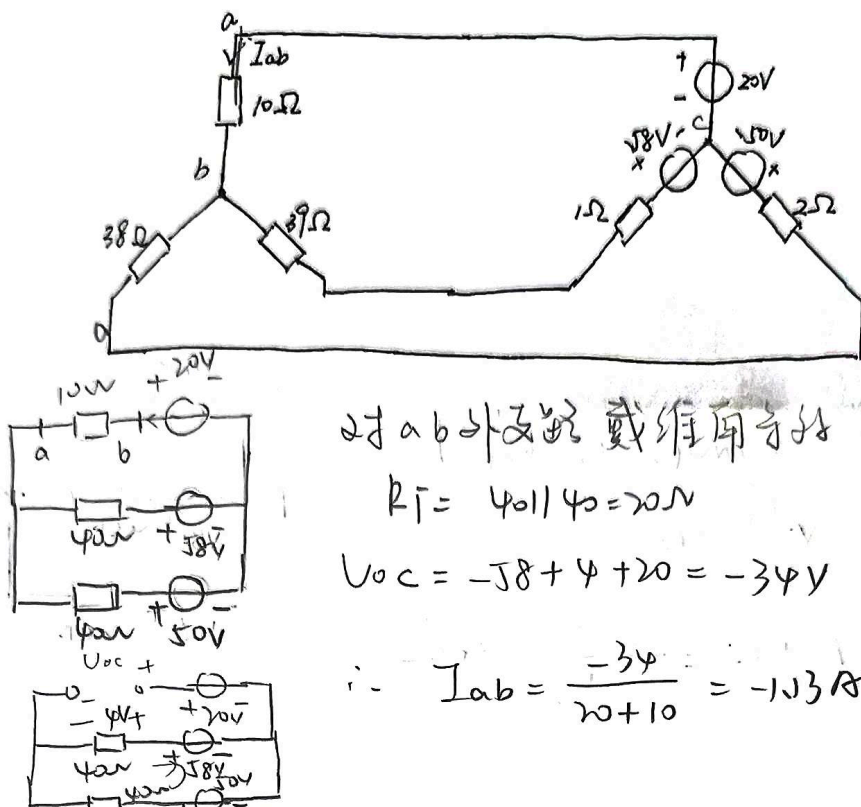

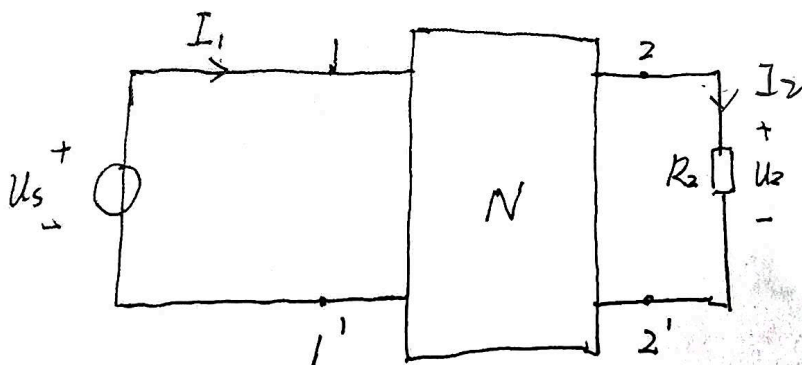4. 题图 3-4 所示电路中, N 为无源线性电阻网络。当 $R_2 = 2\Omega$, $U_s = 6V$ 时, 测得 $I_1 = 2A$,

$U_2 = 2V$ 。如果当 $R_2 = 4\Omega$, $U_s = 10V$ 时, 又测得 $I_1 = 3A$, 求此时的 U_2 。



$$R_2 = 2\Omega \quad U_s = 6V \quad I_1 = 2A \quad U_2 = 2V \quad I_2 = \frac{2}{2} = 1A$$

$$R_2 = 4\Omega \quad U_s' = 10V \quad I_1' = 3A \quad U_2' = ? \quad I_2' = \frac{U_2'}{4}$$

$$U_s'(-I_1') + U_2' I_2 = U_s(-I_1) + U_2(I_2)$$

$$6 \times (-3) + 2 \times \frac{U_2'}{4} = 10 \times (-2) + U_2' \times 1$$

$$U_2' = 4V$$