


1. 如图 4-1 所示电路, $u_s = 50 \cos \omega t$ V, $i_s = 2 \sin \omega t$ A, 其中 $\omega = 2000 \text{ rad/s}$. 计算稳态电流 i .

$$\dot{U}_s = 50 \angle 0^\circ \text{ V}$$

$$\dot{I}_s = 2 \angle -90^\circ = -j2 \text{ A}$$

$$Z_C = -j25 \Omega$$

$$Z_L = j\omega L = j80 \Omega$$

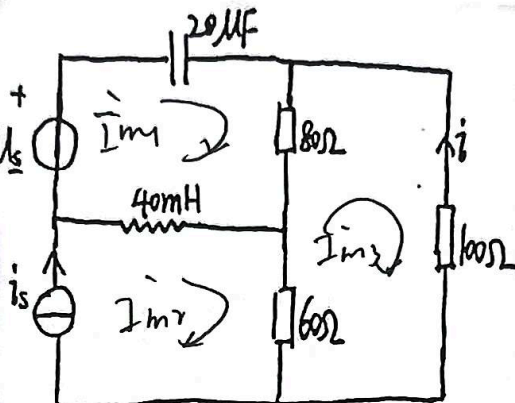


$$\begin{cases} (80 + j55) \dot{I}_{m1} - j80 \dot{I}_{m2} - 80 \dot{I}_{m3} = 50 \\ -80 \dot{I}_{m1} - 60 \dot{I}_{m2} + j40 \dot{I}_{m3} = 0 \\ \dot{I}_{m2} = \dot{I}_s = -j2 \end{cases}$$

$$\dot{I} = -\dot{I}_{m3} = 1.38 \angle 111.81^\circ$$

$$i = 1.38 \cos(2000t + 111.81^\circ)$$

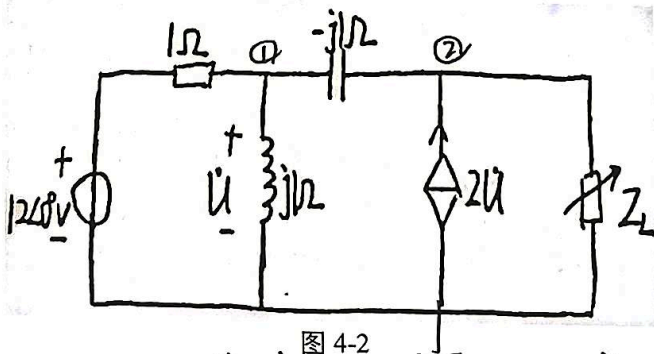2. 如图 4-2 所示电路, Z_L 任意可调。(1) 确定 Z_L 为何值时获得的有功功率最大, 并求此最大有功功率。(2) 若将 Z_L 改为电阻负载 R_L , 再求最大有功功率。




求 $\dot{U}_{oc}$:

$$\left(\frac{1}{1} + \frac{1}{j1} + \frac{1}{-j1}\right) \dot{U}_{m1} - \frac{1}{j1} \dot{U}_{m2} = 12$$

$$-\frac{1}{j1} \dot{U}_{m1} + \left(\frac{1}{-j1}\right) \dot{U}_{m2} = 2$$

$$\dot{U}_{oc} = (6 + j18) \text{ V}$$

求 Z_i : 外加电压源 $\dot{U}_s$ 独立源置零

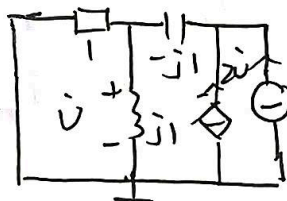

$$\frac{\dot{U}_s}{(1 + j1) - j1} = 2\dot{U} + \dot{I}_s$$



$$\dot{U} = \frac{(1 + j1)}{(1 + j1) - j1} \dot{U}_s$$

$$Z_i = \frac{\dot{U}_s}{\dot{I}_s} = \frac{1}{2} + j\frac{1}{2} \Omega$$

1) $Z_L = 0.5 - j0.5 \Omega$ 时 $P_{max} = 180 \text{ W}$

2) $Z_L = \frac{\sqrt{2}}{2} \Omega$ 时 $P_{max} = 149.12 \text{ W}$

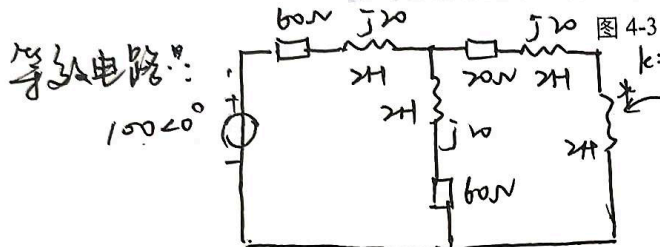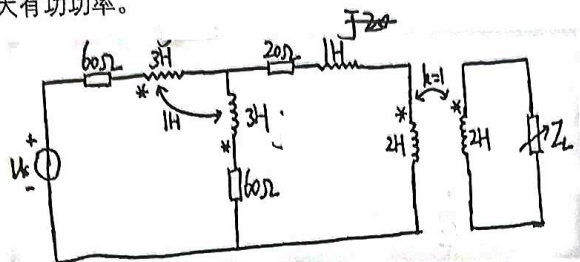3. 如图 4-3 所示电路, $u_s = 100\sqrt{2}\sin 10t$ V, Z_L 任意可调。确定 Z_L 为何值时获得的有功功率最大, 并求此最大有功功率。



$$k = \frac{M}{\sqrt{L_1 L_2}} = 1 = \frac{M}{\sqrt{2 \times 2}}$$

$$\therefore M = 2H$$



将左侧电路等效到右侧

$$Z_{eq} = Z_r + j\omega L_2 = \frac{(100)^2}{50 + j60 + j20} + j\omega L_2 = \frac{(120)^2}{50 + j80} + j20 = j16 + 40$$

$$\therefore Z_L = 40 - j16 \text{ 时 } P_{max}. \text{ 再将右侧电路等效到左侧 } Z_{eq} = \frac{(100)^2}{40 - j16 + j20} + j\omega L_1 = 50 - j30$$

4. 如图 4-4 所示电路中的容抗 X_C 和匝数比 n 分别为多少时可以使 Z_F 获得最大功率, 并求此最大功率, 设 $Z_F = (80 + j60)\Omega$

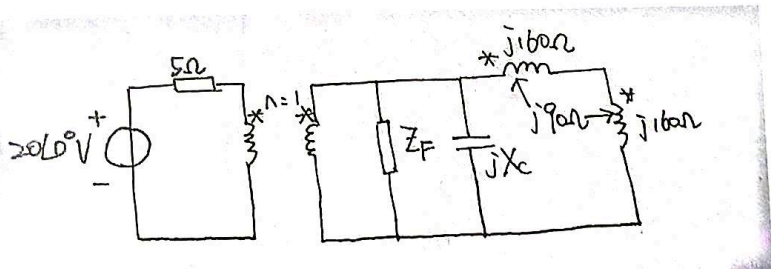


图 4-4

$$\text{右侧 } Z_L = j\omega L_1 + j\omega L_2 + 2j\omega M = j(160 + 160 + 2 \times 90) = j500\Omega$$

$$\text{副边导纳 } Y = \frac{1}{80 + j60} + \frac{1}{jX_C} + \frac{1}{j500} = 0.008 + j(\frac{1}{X_C} - 0.008)$$

$$\text{等效到原边 } Z_1 = n^2 Z = \frac{n^2}{Y} \quad -\frac{1}{X_C} - 0.008 = 0 \text{ 时 } X_C = -125\Omega \quad P_{max}$$

$$Z_1 = n^2 \cdot 125 = 5\Omega \text{ 时 } n = 0.2$$

$$\therefore n = 0.2 \quad X_C = -125\Omega \quad P_{max} = \frac{20^2}{4 \times 5} = 20W$$

$$\dot{U}_C = \frac{1}{2} \dot{U}_S = 50V$$

$$P = \frac{50^2}{4 \times 50} = 125W$$

5. 用节点法列写图 4-5 中所示电路的相量方程


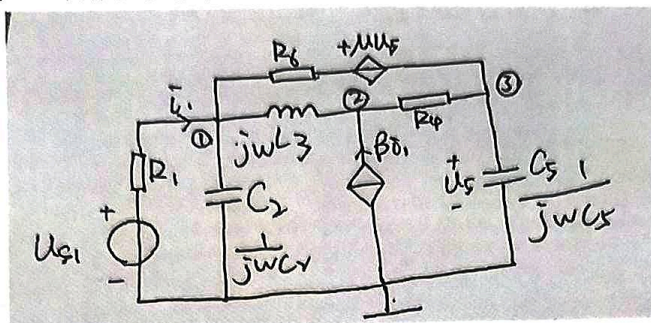


图 4-5

$$\begin{cases} \left(\frac{1}{R_1} + \frac{1}{R_6} + \frac{1}{j\omega L_3} + j\omega C_2 \right) \dot{U}_{n1} - \frac{1}{j\omega L_3} \dot{U}_{n2} - \frac{1}{R_6} \dot{U}_{n3} = \frac{\mu \dot{U}_S}{R_6} + \frac{\dot{U}_{S1}}{R_1} \\ -\frac{1}{j\omega L_3} \dot{U}_{n1} + \left(\frac{1}{j\omega L_3} + \frac{1}{R_4} \right) \dot{U}_{n2} - \frac{1}{R_4} \dot{U}_{n3} = \beta \bar{I}_1 \\ -\frac{1}{R_6} \dot{U}_{n1} - \frac{1}{R_4} \dot{U}_{n2} + \left(\frac{1}{R_4} + \frac{1}{R_6} + j\omega C_5 \right) \dot{U}_{n3} = -\frac{\mu \dot{U}_S}{R_6} \\ \dot{U}_S = \dot{U}_{n3} \\ \bar{I}_1 = \frac{U_{S1} - U_{n1}}{R_1} \end{cases}$$

6. 求出图 4-6 中等效阻抗 Z_i

$$Z_i = (11.92 - j4.62) \Omega$$

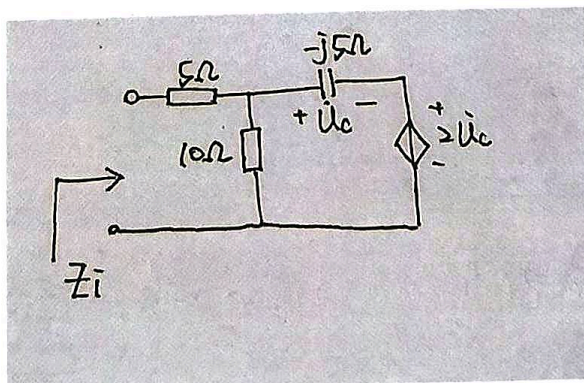

$$\dot{I} = \frac{3\dot{U}_c}{10} + \frac{\dot{U}_c}{-j5} = \dot{U}_c \left(\frac{3+j2}{10} \right)$$

$$\dot{U} = \dot{I} \cdot 5 + 3\dot{U}_c = \frac{9+j2}{2} \dot{U}_c$$

$$Z_i = \frac{5(9+j2)}{3+j2} = (11.92 - j4.62) \Omega$$